

Bilkent University Electrical and Electronics Department

EE102-03 Lab 2 Report: Arithmetic Logic Unit (ALU)

Cankut Bora Tuncer – 22001770

Purpose:

The purpose of this lab was to design an arithmetic logic unit (ALU) capable of performing at least one bitwise and one shift operation via VHDL. The mathematical functions are: summation, multiplication, subtraction, comparison, barrel-shifter, XNOR, AND, OR gates. The VHDL code is designed in a modular fashion. At the end of the lab, the code would be implemented on the Basys3.

Methodology:

The initial task was to decide which eight operations to choose from and how many bits to functionalize. It is decided to use two 3-bit unsigned numbers, in_a and in_b. After deciding on the functionalities, another essential task was implementing the switching operation to toggle between 8 processes. RTL schematic is used to visualize disconnections between pins and test if the pins are driven appropriately. The test bench is initialized to verify that all of the eight operations are working accordingly, and the waveform is recorded.

The constraint file is created, and the bitstream is generated. For the final step, the functions are simulated via. switches and LED.

Design Specifications:

There are 3 inputs and 1 output. The user first selects which operation to implement by inputting the 3 bit input, sel(sel(0), sel(1), sel(2)). Next, the user gives 2 3-bit numbers for in_a(in_a1, in_a2, in_a3) and in_b(in_b1, in_b2, in_b3). The 4 bit output (out_m1, out_m2, out_m3, out_m4) is projected via. LED's.

The VHDL code is constructed in a modular fashion. "main.VHDL" is the top-level module that toggles between user selections and outputs the results of the selected operation.

There are eight sub-modules under the top module:

- summation.vhdl
- multiplication.vhdl
- subtractor.vhdl
- comparator.vhdl
- barrel_shifter.vhdl
- xnorgate.vhdl
- andgate.vhdl
- orgate.vhdl

Furthermore, in order to sustain the modularity of the design, there are two more sub_modules under the above-mentioned sub_modules:

- full_adder.vhdl
- half_adder.vhdl

One possible approach could be including further sub_modules into the adders such as and gate or gate and xor gate, but these gates are already implemented in VHDL. Thus, it is aimed to keep things simple by not creating further sub_modules.

For all but the subtraction operation, it is operated by two 3-bit unsigned numbers. The subtracter inputs two 3-bit signed numbers and outputs one 3-bit signed number. For the multiplication operation, overflow is possible. For future implementations, an overflow detector can be added. For the switching operation, if-else clause is used.

The operations can be summarized as:

SELECT/OPERATION	INPUT/OUTPUT	EXAMPLE
“000” / Summation	$\text{in_a} \ \& \ \text{in_b} / \text{in_a} + \text{in_b}$	“101” + “011” = “1000”
“001” / Multiplication	$\text{in_a} \ \& \ \text{in_b} / \text{in_a} * \text{in_b}$	“111” * “101” = “0011”
“010” / Substraction	$\text{in_a} \ \& \ \text{in_b} / \text{in_a} - \text{in_b}$	“100” - “001” = “011”
“011” / Comparator	$\text{in_a} \ \& \ \text{in_b} / \text{in_a} >, =, < \text{in_b}$	“000” & “111” = “0010”
“100” / Barrel Shifter	$\text{in_a} / \text{“0”} \ \text{in_a3} \ \text{in_a1} \ \text{in_a2}$	“110” = “0011”
“101” / Xnor Gate	$\text{in_a} \ \& \ \text{in_b} / \text{in_a} \ \text{xnor} \ \text{in_b}$	“111” XNOR “011” = “0000”
“110” / And Gate	$\text{in_a} \ \& \ \text{in_b} / \text{in_a} \ \text{and} \ \text{in_b}$	“111” AND “111” = “0001”
“111” / Or Gate	$\text{in_a} \ \& \ \text{in_b} / \text{in_a} \ \text{or} \ \text{in_b}$	“000” OR “000” = “0000”

Figure 1.1 The Operation Table


Results:

The proposed design is first initialized via. VHDL. Due to the complexity of the process, after each creation of a module, the code is simulated with preselected values in the



in b: “111”


in b: “110”

 

For the third input combination:

in_a: "011"

in_b: "101"

 

For the implementation, it is used the Basys3 board. The pin set follows as:

in_a1: V17 switch

out_m(0): U16 LED

in_a2: V16 switch

out_m(1): E19 LED

in_a3: W16 switch

out_m(2): U19 LED

in_b1: W15 switch

out_m(3): V19 LED

in_b2: V15 switch

in_b3: W14 switch

sel(0): U1 switch

sel(1): T1 switch

sel(2): R2 switch

 


Figure 1.3 The Basys3 configuration

In order to verify that the Basys3 implementation is working accordingly, it is chosen 3 different cases from the above mentioned waveform.


Case 1:

in_a: "111"

in_b: "111"

sel: "011"

expected out_m: "0001"

 


Case 2:

in_a: "010"

in_b: "011"

sel: "001"

expected out_m: "0110"

 


Case 3:

in_a: "011"

in_b: "101"

sel: "010"

expected out_m: "110"

 

Conclusion:

In this lab, we implemented an Arithmetic Logic Unit using VHDL and Basys3. Eight different operations are selected, and three 3-bit numbers are inputted into the design, resulting in a 4-bit output. The design is implemented in a modular fashion. During the designing process, there were some design-related problems. For instance, the inputs `in_a` and `in_b` used to drive all the sub_modules in the initial design. This gave a driver error. The inputs are assigned to signals then distributed over the modules, which acted like a buffer to solve it. Also, deciding on the switching algorithm was another hurdle. In conditional assignments, it is not allowed to initialize submodules by port map. Again to overcome this, the outputs from the modules are assigned to unique signals. By using if-else clause, the signals are connected to the final output, `out_m`, using the if-else clause. The design can be improved by increasing the output bit or adding an overflow detector. The waveform and FPGA implementation is working as expected. The VHDL code is implemented on the recent(2021) version of the Vivado; thus the syntax could differ from the older versions.

Appendix:

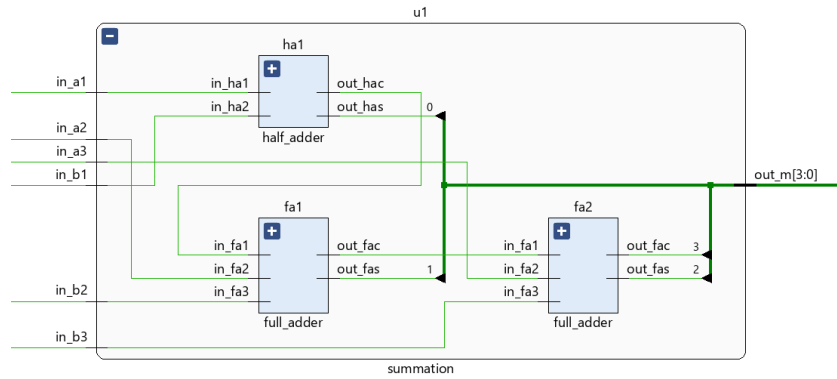


Figure A: Summation Schematic

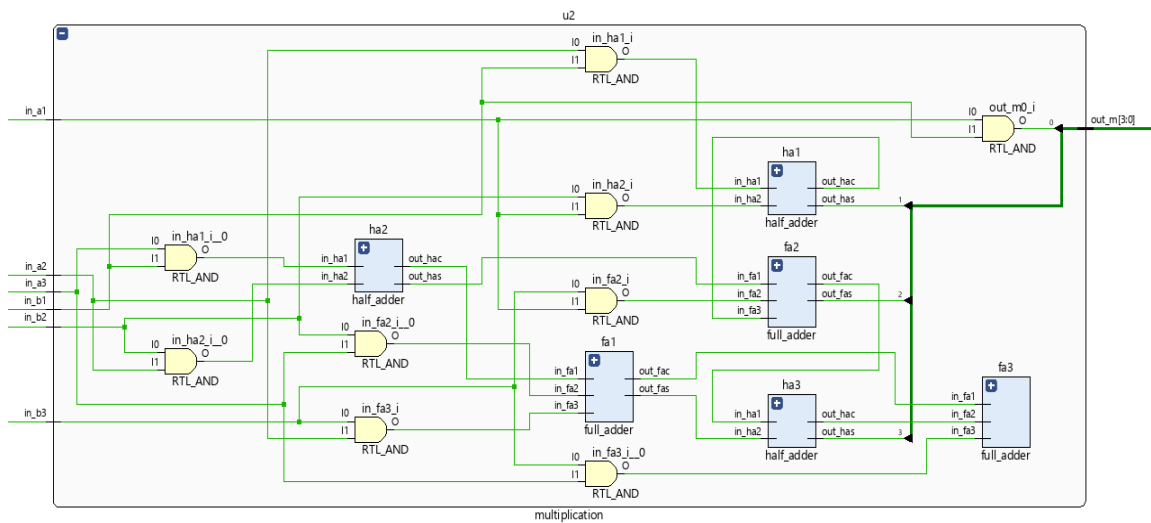


Figure B: Multiplication Schematic

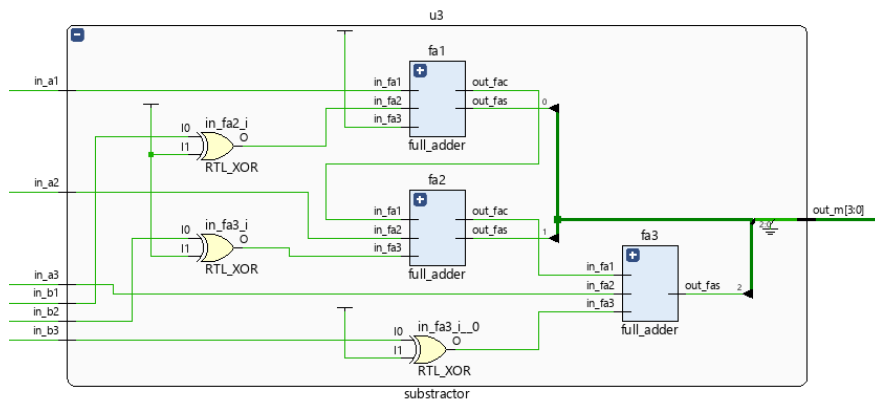


Figure C: Subtraction Schematic

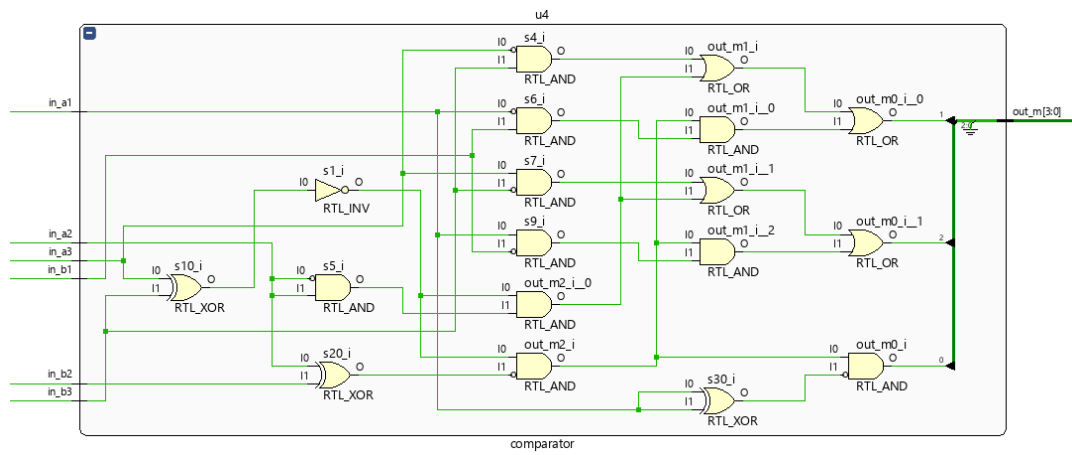


Figure D: Comparator Schematic

 


Figure E: Barrel-Shifter Schematic

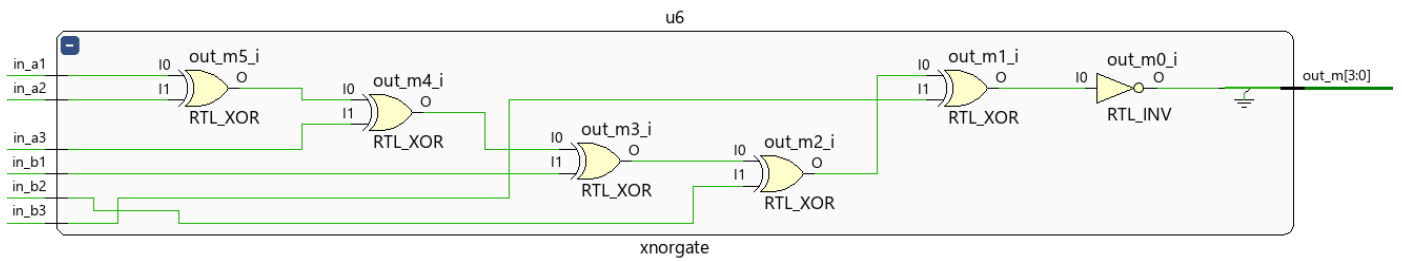


Figure F: Xnor gate Schematic

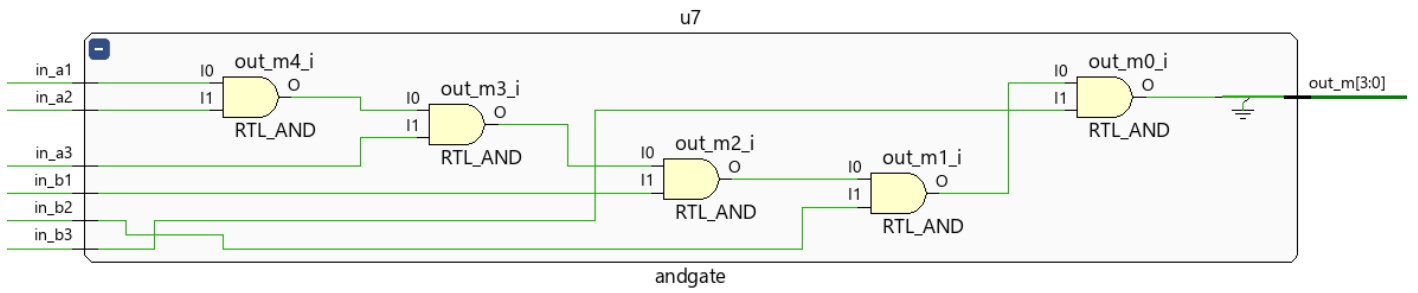


Figure G: And gate Schematic

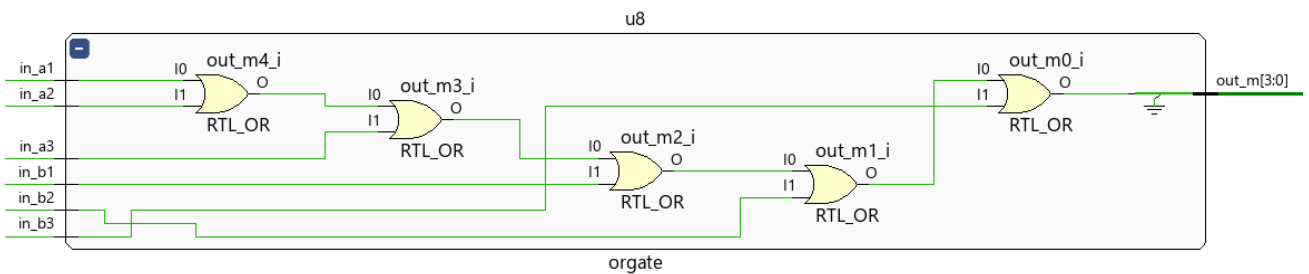


Figure H: Or gate Schematic

main.vhd

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity main is

Port (in_a1,in_a2, in_a3, in_b1, in_b2, in_b3: in STD_LOGIC;

sel: in std_logic_vector(2 downto 0);

out_m: out std_logic_vector(3 downto 0));

end main;

architecture Behavioral of main is

component summation

```
Port ( in_a1,in_a2, in_a3, in_b1, in_b2, in_b3 : in std_logic;  
      out_m: out std_logic_vector(3 downto 0));
```

end component;

component multiplication

```
Port (in_a1,in_a2, in_a3, in_b1, in_b2, in_b3 : in std_logic;  
      out_m: out std_logic_vector(3 downto 0));
```

end component;

component subtractor

```
Port ( in_a1,in_a2, in_a3, in_b1, in_b2, in_b3 : in std_logic;  
      out_m: out STD_LOGIC_vector(3 downto 0));
```

end component;

component comparator

```
Port ( in_a1,in_a2, in_a3, in_b1, in_b2, in_b3 : in std_logic;  
      out_m: out STD_LOGIC_vector(3 downto 0));
```

end component;

component barrel_shifter

```
Port (in_a1,in_a2, in_a3: in std_logic;  
      out_m: out STD_LOGIC_vector(3 downto 0));
```

end component;

component xnorgate

```
Port ( in_a1,in_a2, in_a3, in_b1, in_b2, in_b3 : in std_logic;  
      out_m: out STD_LOGIC_vector(3 downto 0));
```

end component;

component andgate

```
Port ( in_a1,in_a2, in_a3, in_b1, in_b2, in_b3 : in std_logic;
```

```
      out_m: out STD_LOGIC_vector(3 downto 0));
```

end component;

component orgate

```
Port ( in_a1,in_a2, in_a3, in_b1, in_b2, in_b3 : in std_logic;
```

```
      out_m: out STD_LOGIC_vector(3 downto 0));
```

end component;

```
signal ina1,ina2,ina3,inb1,inb2,inb3: std_logic;
```

```
signal out1, out2, out3, out4, out5, out6, out7, out8: std_logic_vector(3 downto 0);
```

begin

```
ina1 <= in_a1;
```

```
ina2 <= in_a2;
```

```
ina3 <= in_a3;
```

```
inb1 <= in_b1;
```

```
inb2 <= in_b2;
```

```
inb3 <= in_b3;
```

u1: summation

```
port map(in_a1 => ina1,in_a2 => ina2, in_a3 => ina3,
```

```
      in_b1 => inb1,in_b2 => inb2, in_b3 => inb3,
```

```
      out_m => out1);
```

u2: multiplication

```
port map(in_a1 => ina1,in_a2 => ina2, in_a3 => ina3,
```

```
      in_b1 => inb1,in_b2 => inb2, in_b3 => inb3,
```

```
out_m => out2);
```

u3: subtractor

```
port map(in_a1 => ina1,in_a2 => ina2, in_a3 => ina3,
```

```
in_b1 => inb1,in_b2 => inb2, in_b3 => inb3,
```

```
out_m => out3);
```

u4: comparator

```
port map(in_a1 => ina1,in_a2 => ina2, in_a3 => ina3,
```

```
in_b1 => inb1,in_b2 => inb2, in_b3 => inb3,
```

```
out_m => out4);
```

u5: barrel_shifter

```
port map(in_a1 => ina1,in_a2 => ina2, in_a3 => ina3,
```

```
out_m => out5);
```

u6: xnorgate

```
port map(in_a1 => ina1,in_a2 => ina2, in_a3 => ina3,
```

```
in_b1 => inb1,in_b2 => inb2, in_b3 => inb3,
```

```
out_m => out6);
```

u7: andgate

```
port map(in_a1 => ina1,in_a2 => ina2, in_a3 => ina3,
```

```
in_b1 => inb1,in_b2 => inb2, in_b3 => inb3,
```

```
out_m => out7);
```

u8: orgate

```
port map(in_a1 => ina1,in_a2 => ina2, in_a3 => ina3,
```

```
in_b1 => inb1,in_b2 => inb2, in_b3 => inb3,
```

```
out_m => out8);
```

```
process(sel, out1, out2, out3, out4, out5, out6, out7, out8)
```

```
begin
```

```
    if sel = "000" then
```

```
        out_m <= out1;
```

```
    elsif sel = "001" then
```

```
        out_m <= out2;
```

```
    elsif sel = "010" then
```

```
        out_m <= out3;
```

```
    elsif sel = "011" then
```

```
        out_m <= out4;
```

```
    elsif sel = "100" then
```

```
        out_m <= out5;
```

```
    elsif sel = "101" then
```

```
        out_m <= out6;
```

```
    elsif sel = "110" then
```

```
        out_m <= out7;
```

```
    elsif sel = "111" then
```

```
        out_m <= out8;
```

```
    else
```

```
        out_m <= "0000";
```

```
    end if;
```

```
end process;
```

```
end Behavioral;
```

```
summation.vhd
```

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- entitiy declare

entity summation is

    Port ( in_a1,in_a2, in_a3, in_b1, in_b2, in_b3 : in STD_LOGIC;

           out_m: out STD_LOGIC_vector(3 downto 0));

end summation;

-- architecture declare

architecture Behavioral of summation is

--half adder module is declared

component half_adder

    Port ( in_ha1 : in STD_LOGIC;

           in_ha2 : in STD_LOGIC;

           out_has : out STD_LOGIC;

           out_hac : out STD_LOGIC);

end component;

--full adder module is declared

component full_adder

    Port ( in_fa1 : in STD_LOGIC;

           in_fa2 : in STD_LOGIC;

           in_fa3 : in STD_LOGIC;

           out_fas : out STD_LOGIC;

           out_fac : out STD_LOGIC);

end component;

```

```

--signal declaration for connections

signal hac,fac1: std_logic;

begin

    ha1:half_adder -- initiating the first half-adder

    port map(in_ha1 => in_a1, in_ha2 => in_b1,

        out_has => out_m(0), out_hac => hac);

    fa1:full_adder -- initiating the first full-adder

    port map(in_fa1 => hac, in_fa2 => in_a2, in_fa3 => in_b2,

        out_fas => out_m(1), out_fac => fac1);

    fa2:full_adder -- initiating the second full-adder

    port map(in_fa1 => fac1, in_fa2 => in_a3, in_fa3 => in_b3,

        out_fas => out_m(2), out_fac => out_m(3));

end Behavioral;

```

multiplication.vhd

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- entitiy declare

entity multiplication is

    Port (in_a1,in_a2, in_a3, in_b1, in_b2, in_b3 : in STD_LOGIC;

        out_m: out STD_LOGIC_vector(3 downto 0));

end multiplication;

-- architecture declare

architecture Behavioral of multiplication is

```



```

--half adder module is declared

component half_adder

    Port ( in_ha1 : in STD_LOGIC;

           in_ha2 : in STD_LOGIC;

           out_has : out STD_LOGIC;

           out_hac : out STD_LOGIC);

end component;

--full adder module is declared

component full_adder

    Port ( in_fa1 : in STD_LOGIC;

           in_fa2 : in STD_LOGIC;

           in_fa3 : in STD_LOGIC;

           out_fas : out STD_LOGIC;

           out_fac : out STD_LOGIC);

end component;

--signal declaration for connections

signal sum1,sum2: std_logic;

signal carry1,carry2,carry3,carry4,carry5: std_logic;

signal dump2,dump3: std_logic;

signal sel: std_logic;

begin

out_m(0) <= in_a1 and in_b1;

ha1: half_adder -- initiating the first half-adder

port map(in_ha1 => (in_a2 and in_b1), in_ha2 =>(in_b2 and in_a1),

```

```

        out_has => out_m(1), out_hac => carry1);

ha2: half_adder -- initiating the second half-adder

port map(in_ha1 => (in_a3 and in_b1), in_ha2 =>(in_b2 and in_a2),

        out_has => sum1, out_hac => carry2);

fa1: full_adder -- initiating the first full-adder

port map(in_fa1 => carry2, in_fa2 =>(in_b2 and in_a3), in_fa3 => (in_b3 and in_a2),

        out_fas => sum2, out_fac => carry3);

fa2: full_adder -- initiating the second full-adder

port map(in_fa1 => sum1, in_fa2 =>(in_b3 and in_a1), in_fa3 => carry1,

        out_fas => out_m(2), out_fac => carry4);

ha3: half_adder -- initiating the third half-adder

port map(in_ha1 => carry4, in_ha2 =>sum2,

        out_has => out_m(3), out_hac => carry5);

fa3: full_adder -- initiating the third full-adder

port map(in_fa1 => carry3, in_fa2 =>carry5, in_fa3 => (in_b3 and in_a3),

        out_fas => dump2, out_fac => dump3);

end Behavioral;

```

subtractor.vhd

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- entitiy declare

entity subtractor is

    Port ( in_a1,in_a2, in_a3, in_b1, in_b2, in_b3 : in STD_LOGIC;

        out_m: out STD_LOGIC_vector(3 downto 0));

```

```

end subtractor;

-- architecture declare

architecture Behavioral of subtractor is

--full adder module is declared

component full_adder

    Port ( in_fa1 : in STD_LOGIC;

          in_fa2 : in STD_LOGIC;

          in_fa3 : in STD_LOGIC;

          out_fas : out STD_LOGIC;

          out_fac : out STD_LOGIC);

end component;

--signal declaration for connections

signal dummy,fac1,fac2: std_logic;

begin

    fa1:full_adder -- initiating the first full-adder

    port map(in_fa1 => in_a1, in_fa2 => (in_b1 xor '1'), in_fa3 => '1',

            out_fas => out_m(0), out_fac => fac1);

    fa2:full_adder -- initiating the second full-adder

    port map(in_fa1 => fac1, in_fa2 => in_a2, in_fa3 => (in_b2 xor '1'),

            out_fas => out_m(1), out_fac => fac2);

    fa3:full_adder -- initiating the third full-adder

    port map(in_fa1 => fac2, in_fa2 => in_a3, in_fa3 => (in_b3 xor '1'),

            out_fas => out_m(2), out_fac => dummy);

    out_m(3) <= '0';

```

```
end Behavioral;
```

comparator.vhd

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- entitiy declare
```

```
entity comparator is
```

```
    Port ( in_a1,in_a2, in_a3, in_b1, in_b2, in_b3 : in STD_LOGIC;
```

```
          out_m: out STD_LOGIC_vector(3 downto 0));
```

```
end comparator;
```

```
-- architecture declare
```

```
architecture Behavioral of comparator is
```

```
--signal declaration for connections
```

```
signal s1,s2,s3,s4,s5,s6,s7,s8,s9: std_logic;
```

```
begin
```

```
s1 <= not(in_a3 xor in_b3);
```

```
s2 <= not(in_a2 xor in_b2);
```

```
s3 <= not(in_a1 xor in_b1);
```

```
s4 <= (not in_a3) and in_b3;
```

```
s5 <= (not in_a2) and in_b2;
```

```
s6 <= (not in_a1) and in_b1;
```

```
s7 <= in_a3 and (not in_b3);
```

```
s8 <= in_a2 and (not in_b2);
```

```
s9 <= in_a1 and (not in_b1);
```

```
out_m(0) <= s1 and s2 and s3; -- for a equals b.
```

```

out_m(1) <= s4 or (s1 and s5) or (s1 and s2 and s6); --for a less than b
out_m(2) <= s7 or (s1 and s8) or (s1 and s2 and s9); --for a greater than b
out_m(3) <= '0';

end Behavioral;

```

barrel_shifter.vhd

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity barrel_shifter is

    Port (in_a1,in_a2, in_a3: in STD_LOGIC;

          out_m: out STD_LOGIC_vector(3 downto 0));

end barrel_shifter;

architecture Behavioral of barrel_shifter is

    signal a1, a2, a3: std_logic;

    begin

        a1<= in_a1;

        a2<= in_a2;

        a3<= in_a3;


        out_m <= '0' & a2 & a1 & a3;

    end Behavioral;

```

xnorgate.vhd

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity xnorgate is

```

```

Port ( in_a1,in_a2, in_a3, in_b1, in_b2, in_b3 : in STD_LOGIC;

      out_m: out STD_LOGIC_vector(3 downto 0):= "0000");

end xnorgate;

architecture Behavioral of xnorgate is

begin

out_m(3) <= (not(in_a1 xor in_a2 xor in_a3 xor in_b1 xor in_b2 xor in_b3));

end Behavioral;

```

andgate.vhd

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity andgate is

Port ( in_a1,in_a2, in_a3, in_b1, in_b2, in_b3 : in STD_LOGIC;

      out_m: out STD_LOGIC_vector(3 downto 0):= "0000");

end andgate;

architecture Behavioral of andgate is

begin

out_m(3) <= in_a1 and in_a2 and in_a3 and in_b1 and in_b2 and in_b3;

end Behavioral;

```

orgate.vhd

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity orgate is

Port ( in_a1,in_a2, in_a3, in_b1, in_b2, in_b3 : in STD_LOGIC;

      out_m: out STD_LOGIC_vector(3 downto 0):= "0000");

```

end orgate;

architecture Behavioral of orgate is

begin

out_m(3) <= in_a1 or in_a2 or in_a3 or in_b1 or in_b2 or in_b3;

end Behavioral;

half_adder.vhd

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity half_adder is

Port (in_ha1 : in STD_LOGIC;

in_ha2 : in STD_LOGIC;

out_has : out STD_LOGIC;

out_hac : out STD_LOGIC);

end half_adder;

architecture Behavioral of half_adder is

begin

out_has <= in_ha1 xor in_ha2;

out_hac <= in_ha1 and in_ha2;

end Behavioral;

full_adder.vhd

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity full_adder is

Port (in_fa1 : in STD_LOGIC;

```

    in_fa2 : in STD_LOGIC;

    in_fa3 : in STD_LOGIC;

    out_fas : out STD_LOGIC;

    out_fac : out STD_LOGIC);

end full_adder;

architecture Behavioral of full_adder is

begin

    out_fas <= in_fa1 xor in_fa2 xor in_fa3;

    out_fac <= (in_fa1 and in_fa2) or (in_fa1 and in_fa3) or (in_fa2 and in_fa3);

end Behavioral;

```

testBench_main.vhd

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity testBench_main is

end testBench_main;

architecture Behavioral of testBench_main is

component main

    Port (in_a1,in_a2, in_a3, in_b1, in_b2, in_b3: in STD_LOGIC;

        sel: in std_logic_vector(2 downto 0);

        out_m: out STD_LOGIC_vector(3 downto 0));

end component;

    signal in_a1, in_a2,in_a3,in_b1,in_b2,in_b3: std_logic;

    signal sel: std_logic_vector(2 downto 0);

    signal out_m: std_logic_vector(3 downto 0);

```



```
begin
```

```
    u1: main
```

```
    Port map(in_a1 => in_a1, in_a2 => in_a2, in_a3 => in_a3, in_b1 => in_b1, in_b2 =>  
in_b2, in_b3 => in_b3, sel => sel, out_m =>out_m);
```

```
testBench_main: process
```

```
begin
```

```
    sel <= "000";
```

```
    in_a1 <= '0';
```

```
    in_a2 <= '0';
```

```
    in_a3 <= '0';
```

```
    in_b1 <= '0';
```

```
    in_b2 <= '0';
```

```
    in_b3 <= '0';
```

```
    wait for 100ns;
```

```
        sel <= "000";
```

```
        in_a1 <= '1';
```

```
        in_a2 <= '1';
```

```
        in_a3 <= '1';
```

```
        in_b1 <= '1';
```

```
        in_b2 <= '1';
```

```
        in_b3 <= '1';
```

```
    wait for 100ns;
```

```
        sel <= "001";
```

```
        in_a1 <= '1';
```

```
        in_a2 <= '1';
```

```
in_a3 <= '1';  
in_b1 <= '1';  
in_b2 <= '1';  
in_b3 <= '1';  
wait for 100ns;  
sel <= "010";  
in_a1 <= '1';  
in_a2 <= '1';  
in_a3 <= '1';  
in_b1 <= '1';  
in_b2 <= '1';  
in_b3 <= '1';  
wait for 100ns;  
sel <= "011";  
in_a1 <= '1';  
in_a2 <= '1';  
in_a3 <= '1';  
in_b1 <= '1';  
in_b2 <= '1';  
in_b3 <= '1';  
wait for 100ns;  
sel <= "100";  
in_a1 <= '1';  
in_a2 <= '1';
```

```
in_a3 <= '1';  
  
in_b1 <= '1';  
  
in_b2 <= '1';  
  
in_b3 <= '1';  
wait for 100ns;  
  
sel <= "101";  
  
in_a1 <= '1';  
  
in_a2 <= '1';  
  
in_a3 <= '1';  
  
in_b1 <= '1';  
  
in_b2 <= '1';  
  
in_b3 <= '1';  
wait for 100ns;  
  
sel <= "110";  
  
in_a1 <= '1';  
  
in_a2 <= '1';  
  
in_a3 <= '1';  
  
in_b1 <= '1';  
  
in_b2 <= '1';  
  
in_b3 <= '1';  
wait for 100ns;  
  
sel <= "111";  
  
in_a1 <= '1';  
  
in_a2 <= '1';
```

```
in_a3 <= '1';
```

```
in_b1 <= '1';
```

```
in_b2 <= '1';
```

```
in_b3 <= '1';
```

```
wait for 100ns;
```

```
sel <= "000";
```

```
in_a1 <= '0';
```

```
in_a2 <= '1';
```

```
in_a3 <= '0';
```

```
in_b1 <= '1';
```

```
in_b2 <= '1';
```

```
in_b3 <= '0';
```

```
wait for 100ns;
```

```
sel <= "001";
```

```
in_a1 <= '0';
```

```
in_a2 <= '1';
```

```
in_a3 <= '0';
```

```
in_b1 <= '1';
```

```
in_b2 <= '1';
```

```
in_b3 <= '0';
```

```
wait for 100ns;
```

```
sel <= "010";
```

```
in_a1 <= '0';  
in_a2 <= '1';  
in_a3 <= '0';  
in_b1 <= '1';  
in_b2 <= '1';  
in_b3 <= '0';  
wait for 100ns;  
  
sel <= "011";  
  
in_a1 <= '0';  
in_a2 <= '1';  
in_a3 <= '0';  
in_b1 <= '1';  
in_b2 <= '1';  
in_b3 <= '0';  
wait for 100ns;  
  
sel <= "100";  
  
in_a1 <= '0';  
in_a2 <= '1';  
in_a3 <= '0';  
in_b1 <= '1';  
in_b2 <= '1';  
in_b3 <= '0';  
  
wait for 100ns;
```

```
sel <= "101";

in_a1 <= '0';

in_a2 <= '1';

in_a3 <= '0';

in_b1 <= '1';

in_b2 <= '1';

in_b3 <= '0';

wait for 100ns;

sel <= "110";

in_a1 <= '0';

in_a2 <= '1';

in_a3 <= '0';

in_b1 <= '1';

in_b2 <= '1';

in_b3 <= '0';

wait for 100ns;

sel <= "111";

in_a1 <= '0';

in_a2 <= '1';

in_a3 <= '0';

in_b1 <= '1';

in_b2 <= '1';

in_b3 <= '0';
```

wait for 100ns;

sel <= "000";

in_a1 <= '1';

in_a2 <= '1';

in_a3 <= '0';

in_b1 <= '1';

in_b2 <= '0';

in_b3 <= '1';

wait for 100ns;

sel <= "001";

in_a1 <= '1';

in_a2 <= '1';

in_a3 <= '0';

in_b1 <= '1';

in_b2 <= '0';

in_b3 <= '1';

wait for 100ns;

sel <= "010";

in_a1 <= '1';

in_a2 <= '1';

in_a3 <= '0';

in_b1 <= '1';

in_b2 <= '0';

in_b3 <= '1';

wait for 100ns;

sel <= "011";

in_a1 <= '1';

in_a2 <= '1';

in_a3 <= '0';

in_b1 <= '1';

in_b2 <= '0';

in_b3 <= '1';

wait for 100ns;

sel <= "100";

in_a1 <= '1';

in_a2 <= '1';

in_a3 <= '0';

in_b1 <= '1';

in_b2 <= '0';

in_b3 <= '1';

wait for 100ns;

sel <= "101";

in_a1 <= '1';

in_a2 <= '1';

in_a3 <= '0';

in_b1 <= '1';

in_b2 <= '0';

in_b3 <= '1';


```

wait for 100ns;

    sel <= "110";

    in_a1 <= '1';

    in_a2 <= '1';

    in_a3 <= '0';

    in_b1 <= '1';

    in_b2 <= '0';

    in_b3 <= '1';

wait for 100ns;

    sel <= "111";

    in_a1 <= '1';

    in_a2 <= '1';

    in_a3 <= '0';

    in_b1 <= '1';

    in_b2 <= '0';

    in_b3 <= '1';

wait for 100ns;

end process;

end Behavioral;

```

calculatorconstraints.xdc

```

set_property PACKAGE_PIN V17 [get_ports {in_a1}]

    set_property IOSTANDARD LVCMOS33 [get_ports {in_a1}]

set_property PACKAGE_PIN V16 [get_ports {in_a2}]

    set_property IOSTANDARD LVCMOS33 [get_ports {in_a2}]

```

```
set_property PACKAGE_PIN W16 [get_ports {in_a3}]

set_property IOSTANDARD LVCMOS33 [get_ports {in_a3}]

set_property PACKAGE_PIN W15 [get_ports {in_b1}]

set_property IOSTANDARD LVCMOS33 [get_ports {in_b1}]

set_property PACKAGE_PIN V15 [get_ports {in_b2}]

set_property IOSTANDARD LVCMOS33 [get_ports {in_b2}]

set_property PACKAGE_PIN W14 [get_ports {in_b3}]

set_property IOSTANDARD LVCMOS33 [get_ports {in_b3}]

set_property PACKAGE_PIN U1 [get_ports {sel[0]}]

set_property IOSTANDARD LVCMOS33 [get_ports {sel[0]}]

set_property PACKAGE_PIN T1 [get_ports {sel[1]}]

set_property IOSTANDARD LVCMOS33 [get_ports {sel[1]}]

set_property PACKAGE_PIN R2 [get_ports {sel[2]}]

set_property IOSTANDARD LVCMOS33 [get_ports {sel[2]}]

set_property PACKAGE_PIN U16 [get_ports {out_m[0]}]

set_property IOSTANDARD LVCMOS33 [get_ports {out_m[0]}]

set_property PACKAGE_PIN E19 [get_ports {out_m[1]}]

set_property IOSTANDARD LVCMOS33 [get_ports {out_m[1]}]

set_property PACKAGE_PIN U19 [get_ports {out_m[2]}]

set_property IOSTANDARD LVCMOS33 [get_ports {out_m[2]}]

set_property PACKAGE_PIN V19 [get_ports {out_m[3]}]

set_property IOSTANDARD LVCMOS33 [get_ports {out_m[3]}]
```