

Lab 4: Arithmetic Logic Unit

The purpose of the lab is to build an Arithmetic Logic Unit (ALU). An ALU is a combinational circuit that can perform mathematical operations and is an essential building block for most digital devices (https://en.wikipedia.org/wiki/Arithmetic_logic_unit).

- 1) Design an ALU. It should have **eight** functions: **addition**, **subtraction**, and six others of your choice including at least **one bitwise** and **one shift** operation (Check the list on the Wikipedia page). Implement it in VHDL in a modular fashion. Simulate your modules and put the **simulation results** in your report. Generate an **RTL schematic** and explain it briefly in your report. Deploy your ALU on your **FPGA** and display the outputs through LEDs. Show your schematics and working FPGA to your TA to get their approval. Include representative photos of your FPGA in your report.